


→ This is another common question!

• What if you are told to use only NOR of 2 inputs?

You better take this approach to transform any n-input NOR from (6) to 2-input NORs

a	b	c	f
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0
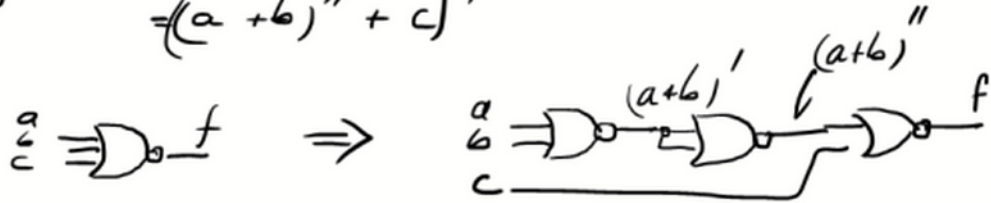
$$f = m_0 = a'b'c' = (a' \cdot b' \cdot c')'' = (a + b + c)' = ((a + b)'' + c)'$$



• What if you are told to use in a circuit only NAND of 2 inputs?


Let's do it the same way: 1) Obtain a circuit like (5) that contains only NAND

2) Let's convert any n-input NAND into a circuit based only in 2-inputs NAND gates

a	b	c	d	f = (abcd)'
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
⋮	⋮	⋮	⋮	⋮
1	1	1	0	1
1	1	1	1	0

$$f = M_{15} = (a' + b' + c' + d')'' = (a \cdot b \cdot c \cdot d)'$$

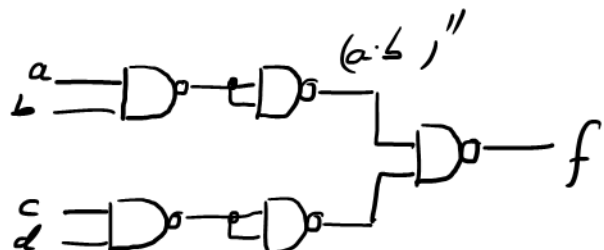
$$f = ((a \cdot b)'' \cdot (c \cdot d)'')'$$



so, up to 5 2-input gates are required to replace a 4-input gate

↑
This 2⁴ combinations
logic function contains only 1 maxterm

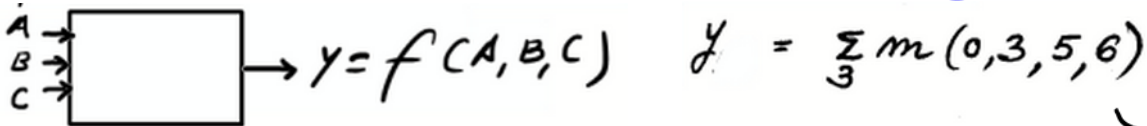This is another example of a circuit using only NAND2 or only NOR2



Example truth table

only NAND

only NOR

Transform n-input NAND to NAND2 and redraw

Transform n-input NOR to NOR2 and redraw


Circuit-A

Circuit-B


$$y = \sum_3 m(0, 3, 5, 6) = (m_0 + m_3 + m_5 + m_6)'' = (A'B'C' + A'BC + ABC' + ABC)''$$

$$y = ((A'B'C') \cdot (A'BC) \cdot (ABC') \cdot (ABC))' \rightarrow \text{Only NAND}$$

3-input NAND

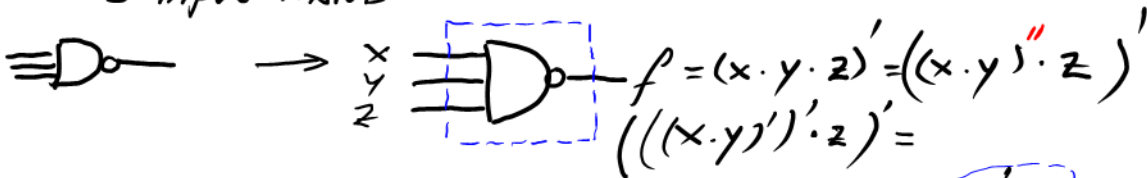


So, it is equivalent to use AND

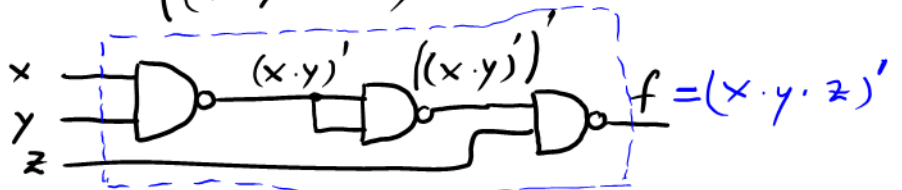

$$y = (m_0'' + m_3'' + m_5'' + m_6'') \rightarrow \text{Circuit only - NOR}$$

$$(A'BC)'' = (A'' + B' + C)' = (A + B' + C')'$$

NOR3 and NOR4

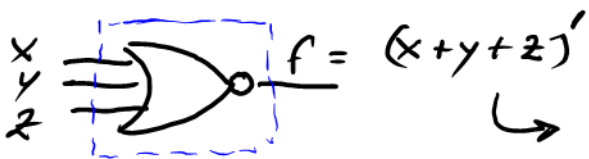

NOR3

$$\begin{aligned} & \rightarrow ((x + y)'' + z)' \\ & \rightarrow (((x + y)')' + z)' \end{aligned}$$

So, it is equivalent to use NOR2

