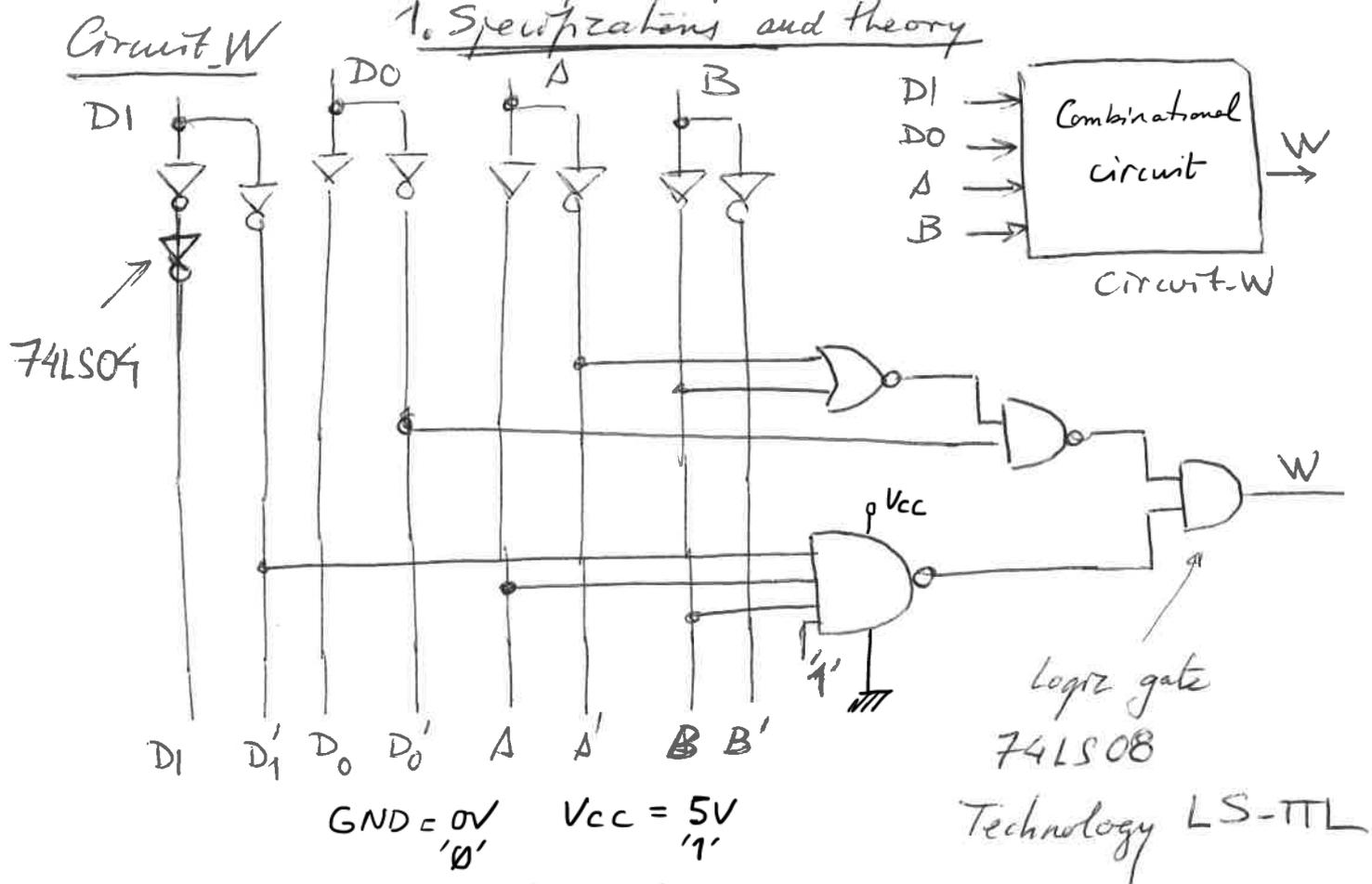


# Tutorial on the analysis of a combinational circuit

## 1. Specifications and theory



→ Objective : Find the truth table

using Proteus virtual laboratory simulator

$$W = f(D_1, D_0, A, B)$$

variables order

$D_1$	$D_0$	$A$	$B$	$W$
0	0	0	0	⋮
0	0	0	1	⋮
			⋮	?
1	1	1	1	

Fill in all the values of the output  $W$

→ Here you can add pages on theory on logic gates and their truth tables, equations and symbols

(This page of specifications can be used 3 times, only changing Proteus simulations by WolframAlpha engine or algebraic equations (Method I) (Method II) (Method III))

# 2. Planning → It is intended to learn about how to use Proteus

Circuit-W

This is for exposing the concepts and the detailed procedure to follow when developing

- Find a similar circuit on the web to copy and adapt
- Project folder `C:\CSD\PS\Lab1_1\Circuit-W\Proteus\`
- Modify the circuit editing gates and wires
- Run the simulation and apply all the combinatorial vectors from "0000" → "1111" and annotate the output in table format (or sum of minterms)
- Compare with your peers to check the result



Truth table

D1	D0	A1B	W
0	0	00	?
		01	⋮
		10	⋮
		11	?

Solve it using method III to study how algebraic functions work.

or product of max terms

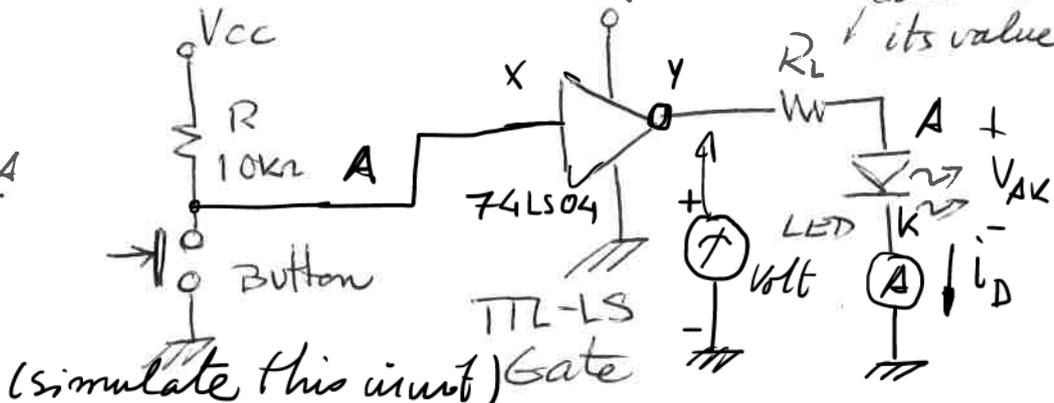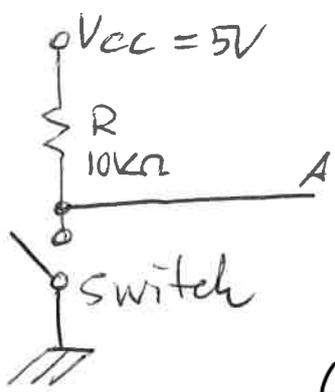- Pay attention to logic families TTL, TTL-LS, HC, HCT,
- Find gates for family TTL-LS → Datasheet of a 74LS08
- Use LED and buttons to apply values and see the outputs. Use a voltmeter to measure




### 3. Development


Here you must paste and comments pictures from the Proteus circuit capture

⇒ DO NOT COPY THE DEVELOPMENT FROM SOMEONE ELSE

⇒ DO IT ALL BY YOURSELF




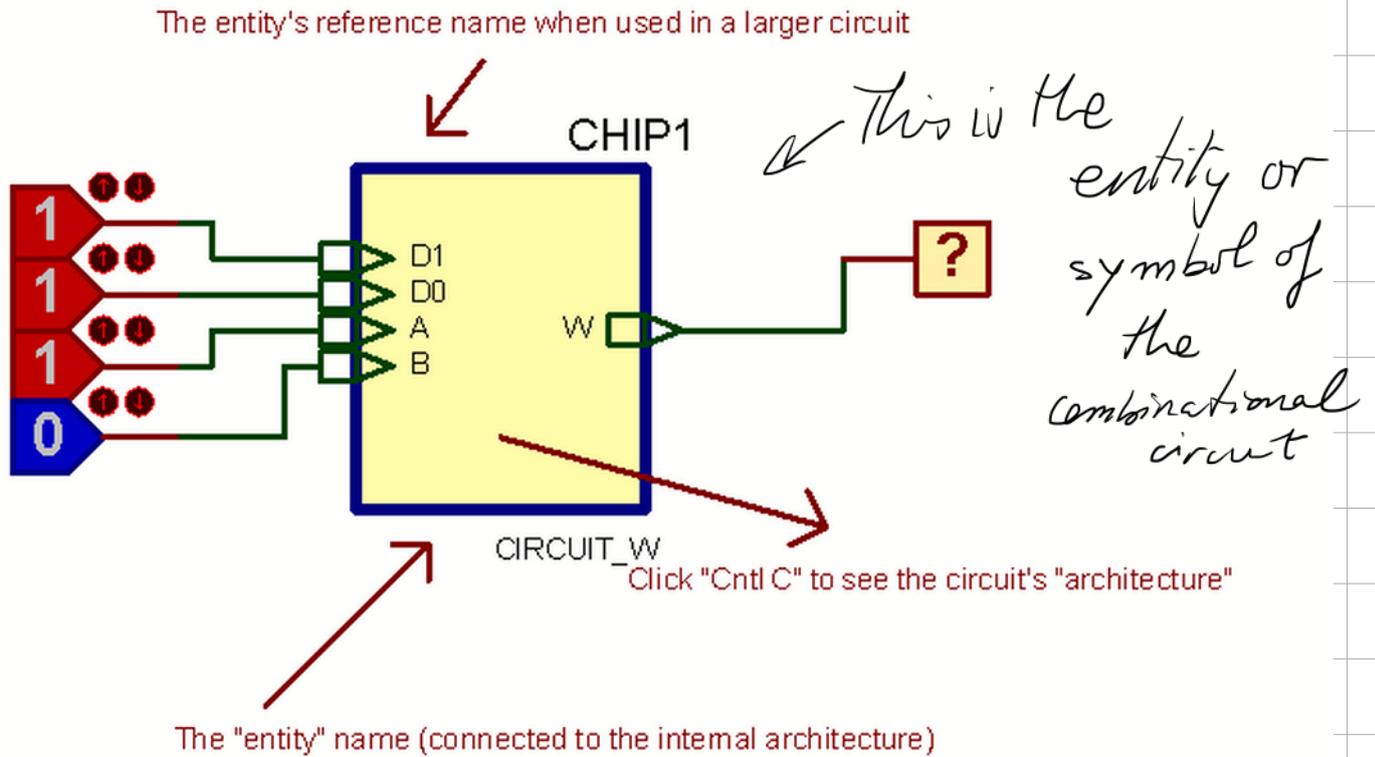


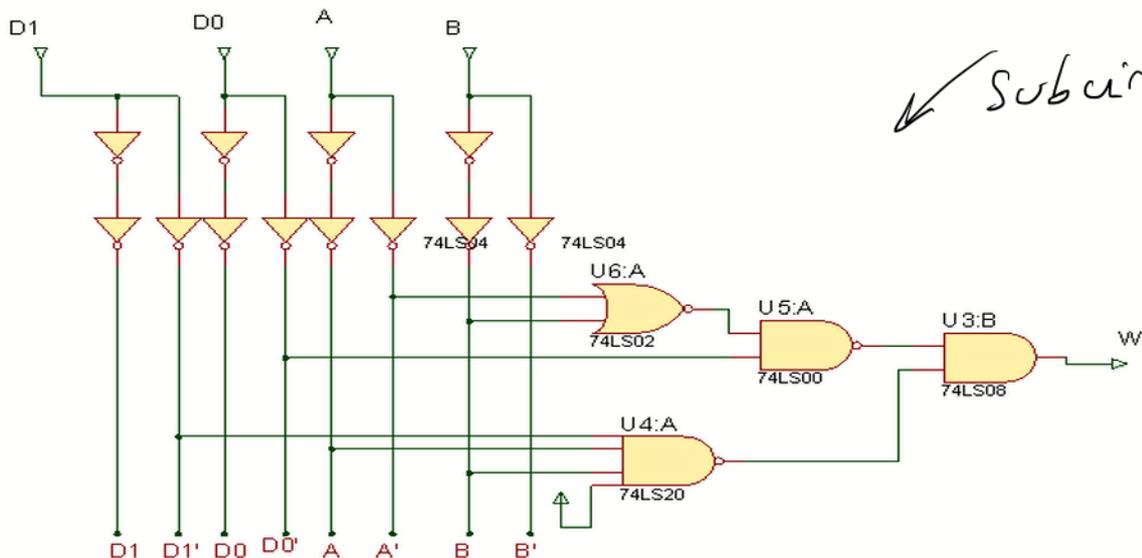This is the circuit's architecture captured in Proteus



This is how the complete truth table is obtained  
→ running simulations for all input combinations.

Decimal value	D1	D0	A	B	W
0	0	0	0	0	1
1	0	0	0	1	1
2	0	0	1	0	0
3	0	0	1	1	0
4	0	1	0	0	1
5	0	1	0	1	1
6	0	1	1	0	1
7	0	1	1	1	0
8	1	0	0	0	1
9	1	0	0	1	1
A	1	0	1	0	0
B	1	0	1	1	1
C	1	1	0	0	1
D	1	1	0	1	1
E	1	1	1	0	1
F	1	1	1	1	1

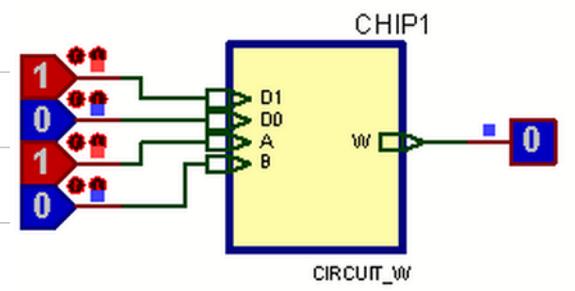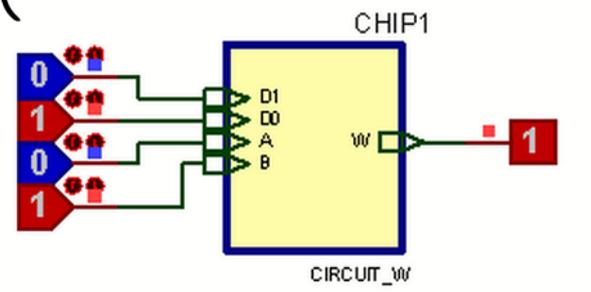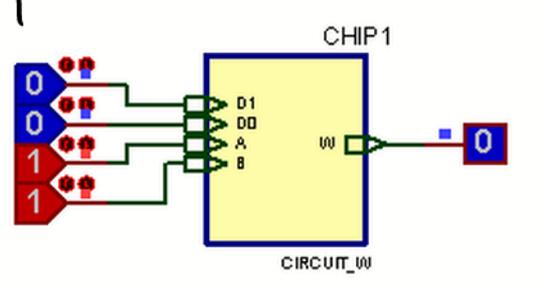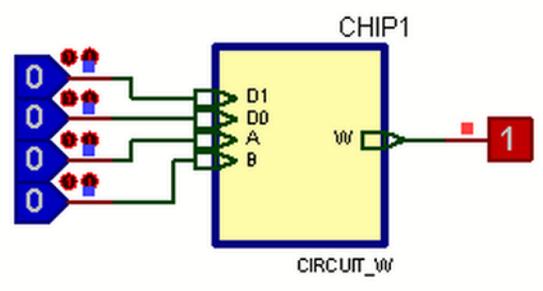

Hexadecimal value

all the combinations

$$W = f(D_1, D_0, A, B) = \prod_4 M(2, 3, 7, 10)$$

## 4. Test and verification

5

You can compare the truth table with other students in class, or with your own results from the analysis in WolframAlpha (method II) or the algebraic analysis using boolean equations (method III).

This method I solution is the same that I got from method III on algebraic equations ✓