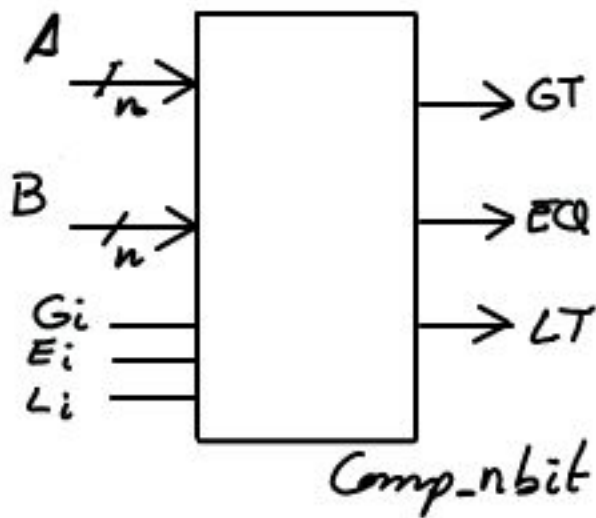


# 1. Specifications

Let's design a Comp-1bit using a flat design based on SoP

Symbol




Truth table

A	B	Gi	Ei	Li	GT	EQ	LT
A > B		x	x	x	1	0	0
A < B		x	x	x	0	0	1
A = B		1	0	0	1	0	0
		0	1	0	0	1	0
		0	0	1	0	0	1

In this way it is possible to chain blocks Comp-1bit to build larger comparators

Thus, for a 1bit comparator we have:

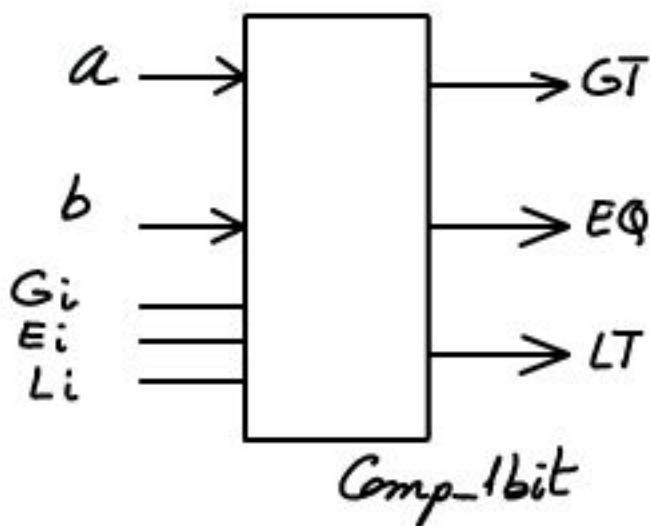

a	b	Gi	Ei	Li	GT	EQ	LT
1	0	x	x	x	1	0	0
0	1	x	x	x	0	0	1
0	0	1	0	0	1	0	0
0	0	0	1	0	0	1	0
0	0	0	0	1	0	0	1
1	1	1	0	0	1	0	0
1	1	0	1	0	0	1	0
1	1	0	0	1	0	0	1

If the bit a=b → the comparison will depend on the previous bits as represented by  $G_i, E_i, L_i$


→ The truth table has  $2^5$  combinations, but many terms are not important because they are impossible like:

(don't care outputs)

$$\begin{matrix} 0 & 1 & 1 & 1 & 0 \\ 1 & 0 & 0 & 1 & 1 \\ 0 & 0 & 0 & 0 & 0 \end{matrix}$$
 here it is impossible to have two '1', etc.

This property will simplify the output logic, and 'Minilog' will detect such incomplete truth table asking for what to do → don't care terms → '-'

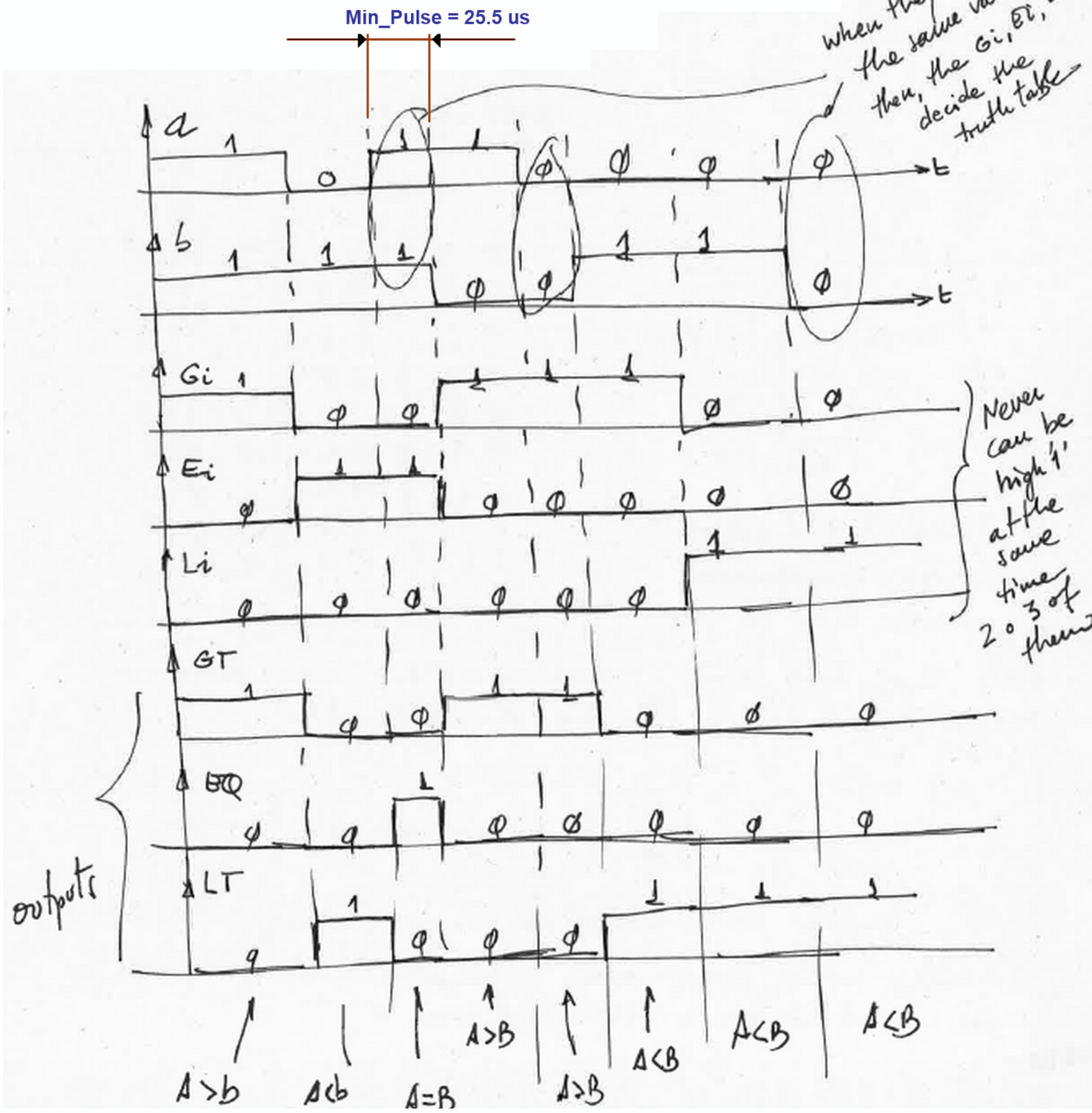This is an example sketch of a timing diagram. In this way you'll be prepared later on to translate it into a VHDL test bench



So that, running the simulator for about 300 us will be enough to test the more meaningful values of the truth table.

## 2. Planning

The idea will be to write the truth table in "minilog" text format, so that we can minimise immediately and obtain the SoP equation.

```
table Comp_1bit
```

```
input A B Gi Ei Li
```

```
output GT EQ LT
```

```
" A B  Gi Ei Li      GT EQ LT
" -----
  1 0  -  -  -      1 0  0  "This is A > B
  0 1  -  -  -      0 0  1  "This is A < B


  0 0  1  0  0      1 0  0  " Because A = B, the chaining inputs decides
  0 0  0  1  0      0 1  0  " Because A = B, the chaining inputs decides
  0 0  0  0  1      0 0  1  " Because A = B, the chaining inputs decides

  1 1  1  0  0      1 0  0  " Because A = B, the chaining inputs decides
  1 1  0  1  0      0 1  0  " Because A = B, the chaining inputs decides
  1 1  0  0  1      0 0  1  " Because A = B, the chaining inputs decides


" There are impossible situation like:
" - -  1  1  1
" - -  1  1  0  which will never occur, and so, they may be a don't care output
"-----
end
```

\* Find this text file in the P4 project on arithmetic circuits
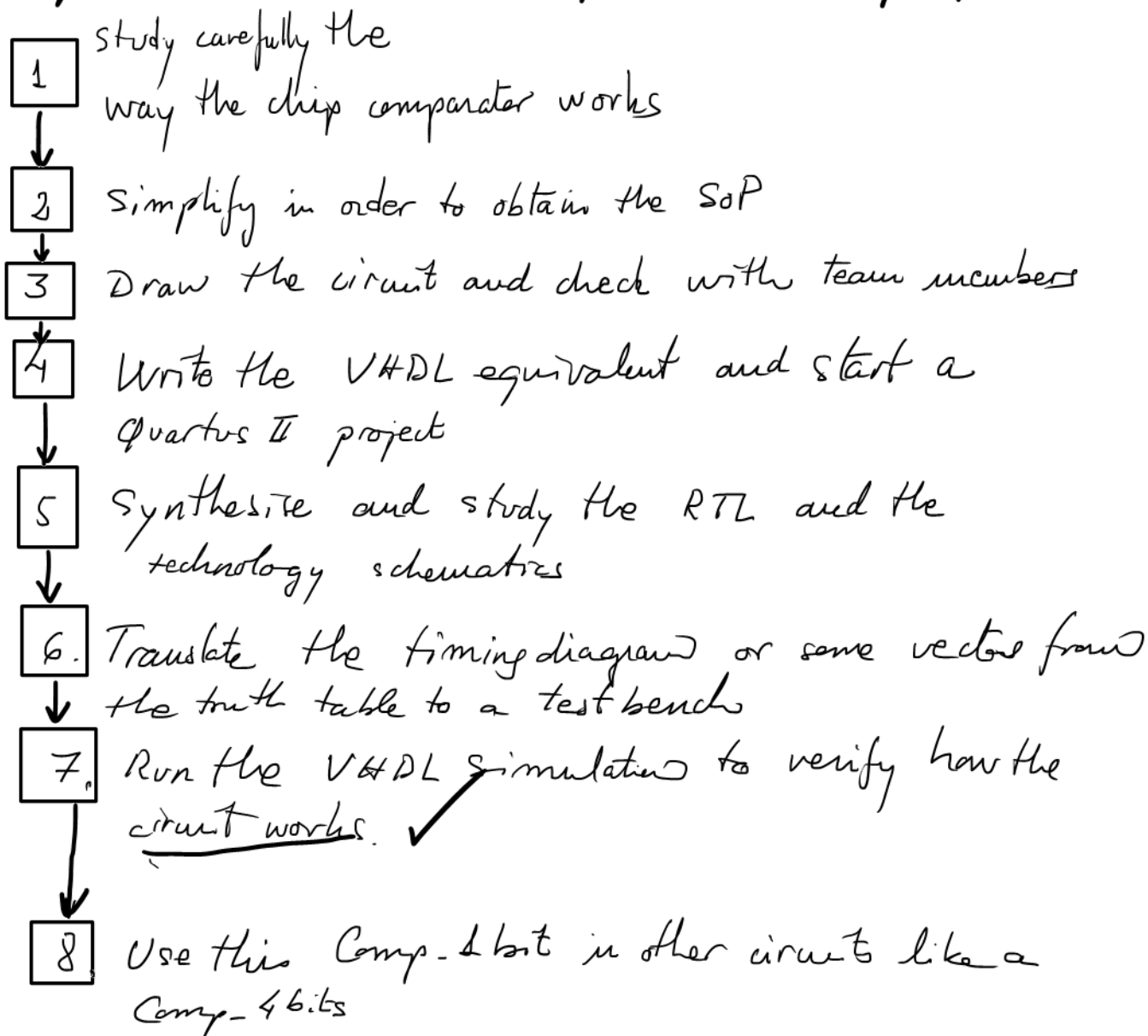
### Example procedure to implement this project



### 3. Development

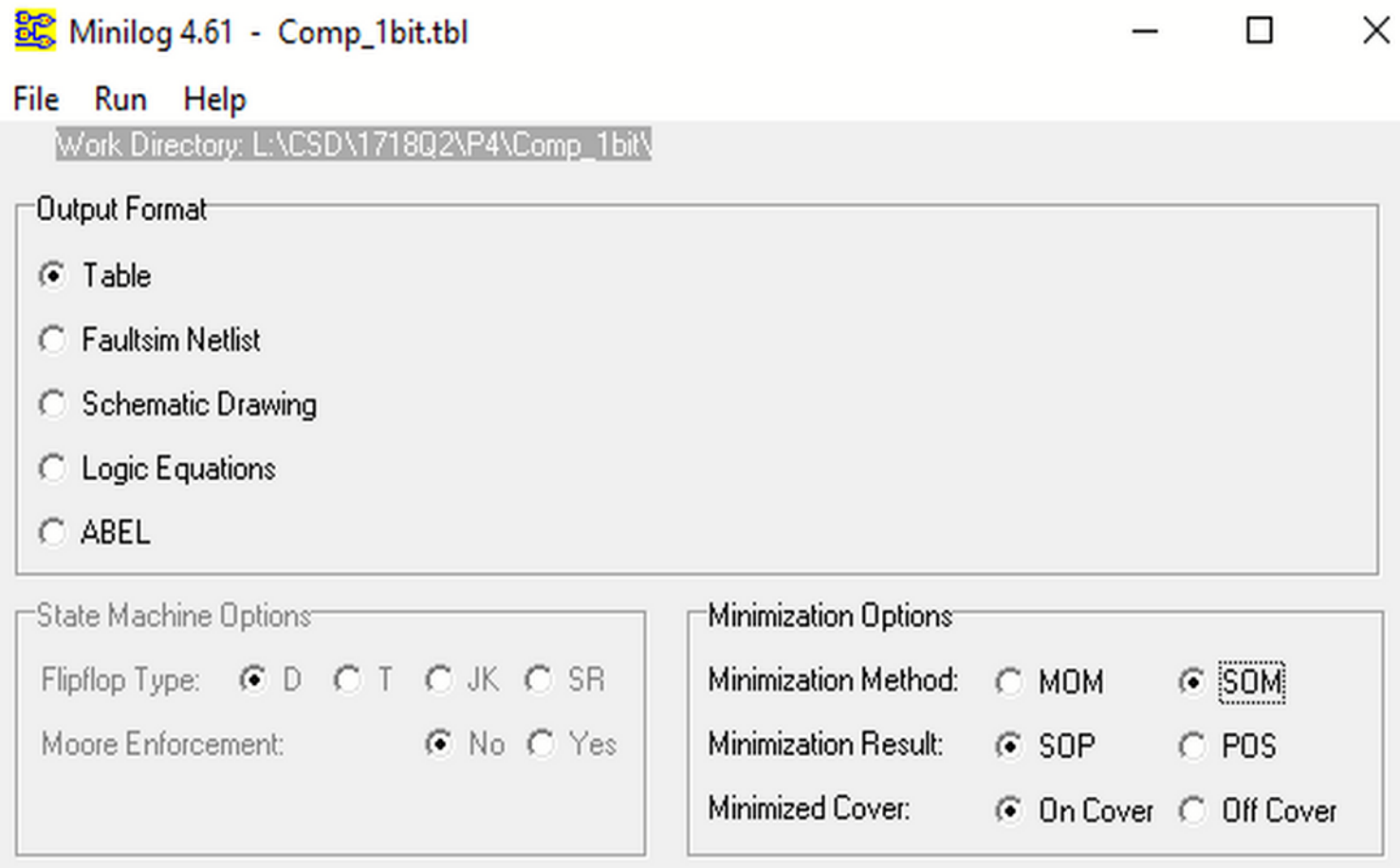


FUNCTION TABLE

GEL	GEL
ABIII	TQT
10---	100
01---	001
00100	100
00010	010
00001	001
11100	100
11010	010
11001	001

The list of impossible terms which we don't care

CHECKING COMPLETENESS OF INPUT TABLE  
INCOMPLETELY SPECIFIED INPUT TABLE; MISSING COVER:

GEL	GEL
ABIII	TQT
00000	???
11000	???
00-11	???
11-11	???
001-1	???
111-1	???
0011-	???
1111-	???

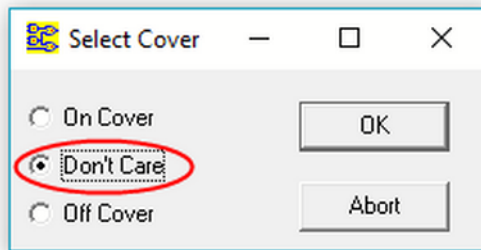

ADD ABOVE TERMS TO ON-/DC-/OFF-COVER OR ABORT PROGRAM  
SELECTED COVER: ( 1 = ON; - = DC; 0 = OFF; Q = Abort ) >

MINIMIZATION RESULT STATISTICS

FOUND 8 ESSENTIAL PRODUCT TERMS  
MAXIMUM FANIN: 6  
TOTAL LITERAL COUNT: 26  
MAXIMUM PRODUCT TERM SIZE: 3  
MAXIMUM OUTPUT FUNCTION SIZE: 3

GEL	GEL
ABIII	TQT
-01--	1..
1-1--	1..
10---	1..
00-1-	.1.
11-1-	.1.
0---1	..1
-1--1	..1
01---	...1


The interpretation of the output format:

Greater than  $GT = A \cdot B' + A \cdot G_i + B' \cdot G_i$

Equal:  $EQ = A' \cdot B' \cdot E_i + A \cdot B \cdot E_i$

Less than:  $LT = B \cdot L_i + A' \cdot L_i + A' \cdot B$

And the equivalent circuit based on SoP

 

Development. Synthesis of the circuit using an EDA tool like Lattice Semiconductor ispLEVER Classic / Intel-Altera Quartus II or Xilinx ISE

This is the VHDL code. The structural equations in SoP from above:

```

-----
-- An example of a 1-bit comparator using described using simplified logic
-- equations (structural) Sum of Products (SoP)
-----
-- Project P4 - CSD : Arithmetic circuits
-- http://digsys.upc.es
-----

LIBRARY ieee;
USE IEEE.STD_LOGIC_1164.all;

ENTITY Comp_1bit IS
  PORT (
    A,B, Gi, Ei, Li : IN STD_LOGIC;
    GT, EQ, LT : OUT STD_LOGIC
  );
END Comp_1bit;

ARCHITECTURE logic_equations_SoP OF Comp_1bit IS
BEGIN


GT <= (not(B) and Gi) or (A and Gi) or (A and not(B));
LT <= (not(A) and Li) or (B and Li) or (B and not(A));
EQ <= (not(A) and not(B) and Ei) or (A and B and Ei);

END logic_equations_SoP;

```

} The block definitions as an entity

} Equations in VHDL in SoP

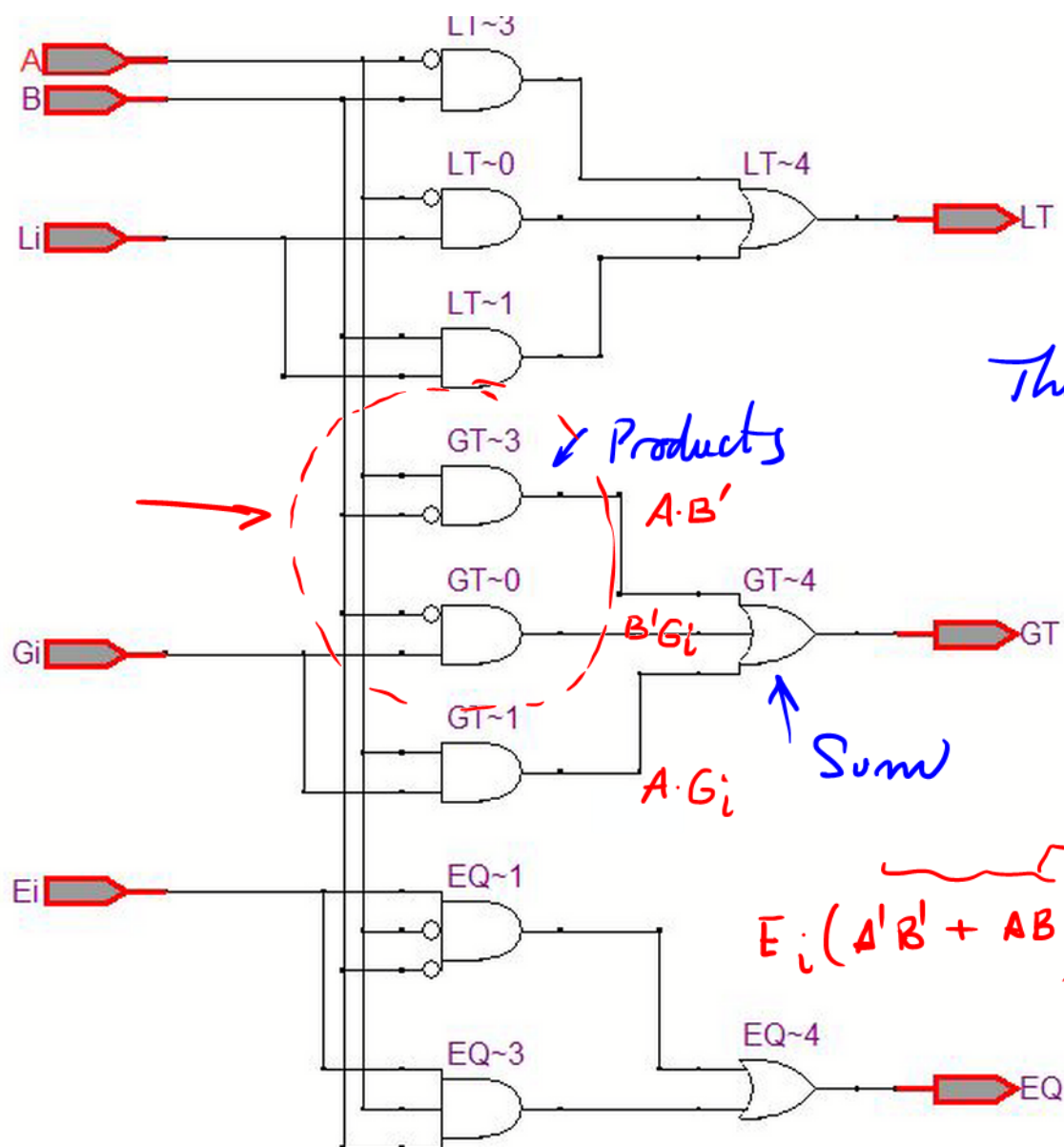

This is the RTL synthesized by Quartus II

Products

$A \cdot B'$

$B' \cdot G_i$

$A \cdot G_i$

Sum

$GT = AB' + B' \cdot G_i + AG_i$


$E_i (A'B' + AB)$

Identity function

A	B	y
0	0	1
0	1	0
1	0	0
1	1	1



$(A \oplus B)'$

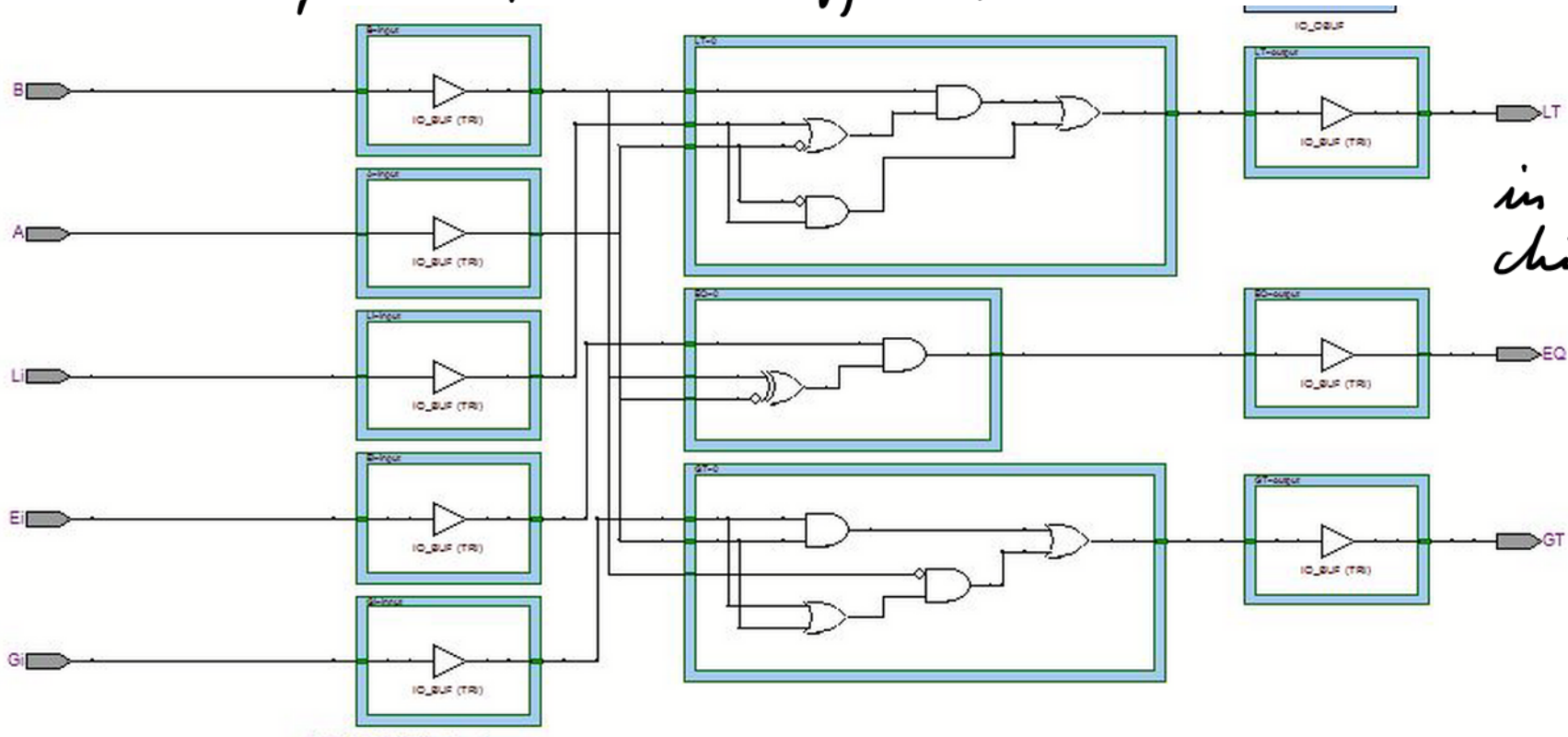This is a picture of the technology view, where you can see the exact logic implemented



logic implemented in the target chip Cyclone III

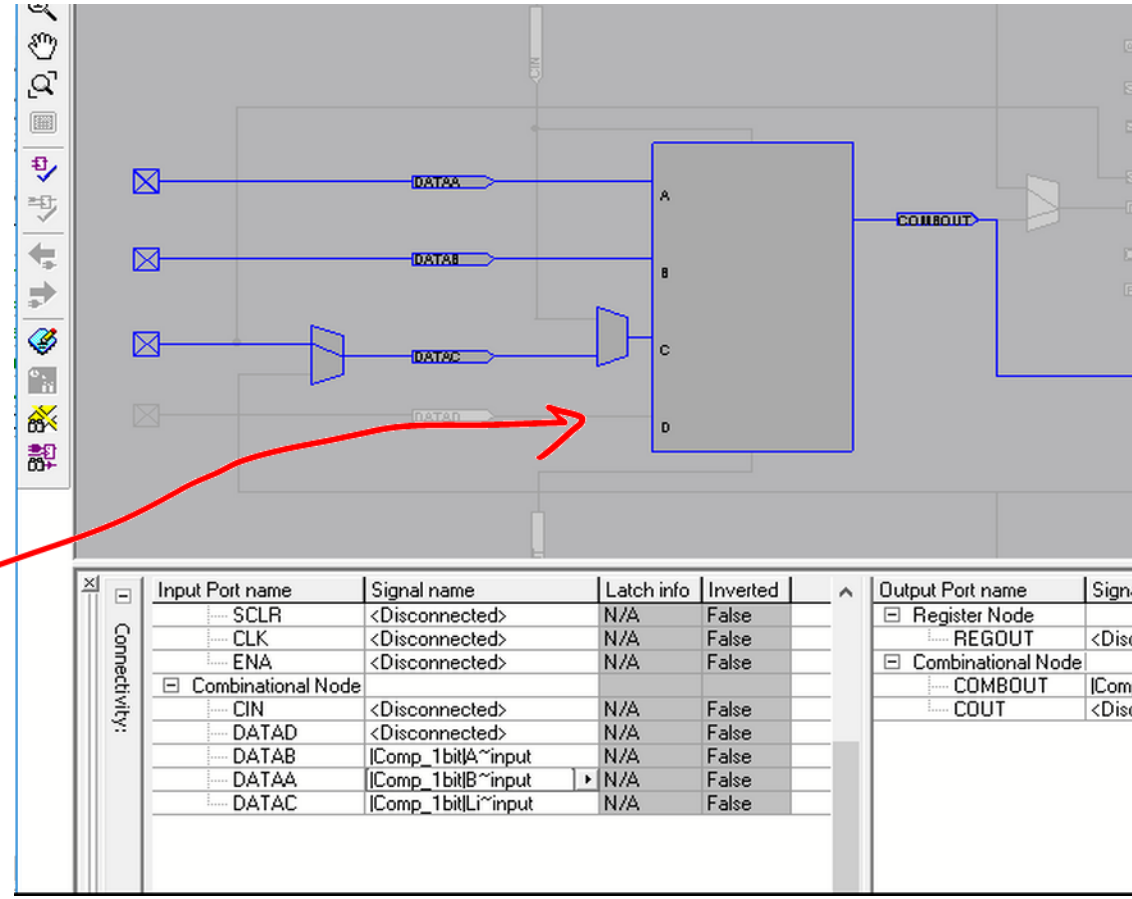 These are some pictures from the chip planner tool




logic element (LE)

There are thousands of them in the Cyclone III

FPGA

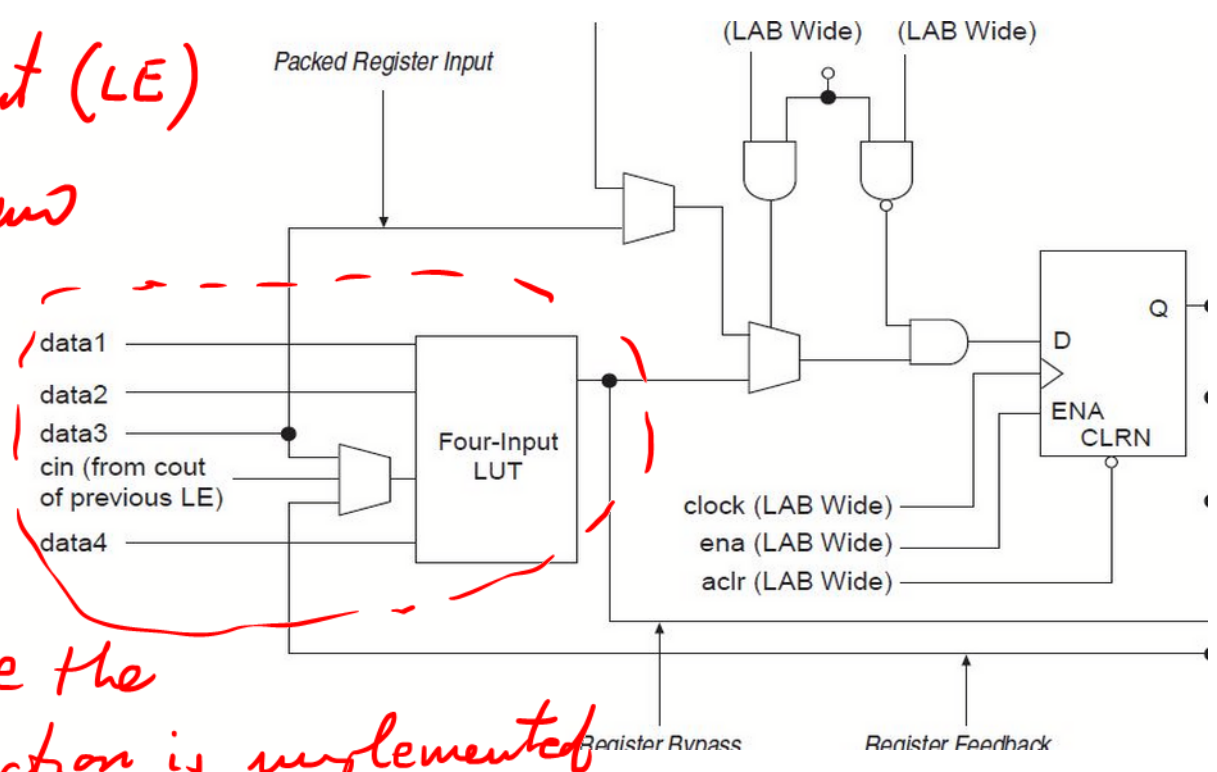This is the combinational LUT of a LE where the logic function is implemented



4. Testing using a VHDL test bench fixture, so that we can apply input stimulus and check the outputs, thus, verifying the circuit's truth table and validating the design of the component.

```
-- *** Test Bench - User Defined Section ***
```

```
tb : PROCESS
BEGIN
-- Circuit initialisation period (do nothing).
wait for 100 ns;
wait for Min_Pulse*1.5;
```

```
-- Let's start the stimulus activity:
A <= '0';      -- This is EQ = 1
B <= '0';

Gi <= '0';
Ei <= '1';
Li <= '0';
```

stimulus of a given vector  
25.5 μs

```
-- constants:
constant Min_Pulse : time := 25.5 us;
-- In this way, for testing several vectors,
-- running the simulator 1000 us will be enough
```

run 1000 us in ModelSim

```
wait for Min_Pulse*1.76;

A <= '1';      -- This is EQ = 1
B <= '1';

Gi <= '0';
Ei <= '1';
Li <= '0';
```

```
wait for Min_Pulse*1.76;

A <= '1';      -- This is GT = 1
B <= '0';

Gi <= '0';
Ei <= '1';
Li <= '0';
```

This situation is wrong, so, the output is not important

