



This is the CC1
combinational circuit to calculate
the next state to go

This is the
CC2
circuit to
calculate the
output Z

State register r=3
D_FF

Discussion on the RTL results