

Problem 1

Ⓐ	E _L	X ₃	X ₂	X ₁	X ₀	Y _{15,L}	Y _{14,L}	Y _{13,L}	Y _{2,L}	Y _{1,L}	Y _{0,L}
disable	1	X	X	X	X	1	1	1	1	1	1
	0	0	0	0	0	1	1	1	1	1	0
	0	0	0	0	1	1	1	1	1	0	1
		⋮							⋱			
	0	1	1	1	0	1	0	1	1	1	1
	0	1	1	1	1	0	1	1	1	1	1

$$Y_{7,L} = f(E_L, X) = (E_L + X_3 + X_2' + X_1' + X_0') = M_7$$

$$Y_{14,L} = M_{14} = (E_L + X_3' + X_2' + X_1' + X_0)$$

The functions in this chip have 31 minterms and only one maxterm

Ⓑ Redraw the truth table in order to make it easier

	A ₃	A ₂	A ₁	A ₀	B ₃	B ₂	B ₁	B ₀
0	0	0	0	0	0	0	0	0
1	0	0	0	1	0	0	0	1
2	0	0	1	0	0	0	1	1
3	0	0	1	1	0	0	1	0
4	0	1	0	0	0	1	1	1
5	0	1	0	1	0	1	1	0
6	0	1	1	0	0	1	0	0
7	0	1	1	1	0	1	0	1
8	1	0	0	0	1	1	1	1
9	1	0	0	1	1	1	1	0
10	1	0	1	0	1	1	0	0
11	1	0	1	1	1	1	0	1
12	1	1	0	0	1	0	0	0
13	1	1	0	1	1	0	0	1
14	1	1	1	0	1	0	1	1
15	1	1	1	1	1	0	1	0

$$B_0 = f(A_3, A_2, A_1, A_0) = \sum_4 m(1, 2, 4, 7, 8, 11, 13, 14)$$

$$m_2 = A_3' A_2' A_1 A_0$$

OR

sum of minterms

$$B1 = f(A3, A2, A1, A0) = \prod M(0, 1, 6, 7, 10, 11, 12, 13)$$


\uparrow
 4
 AND
 product of maxterms OR

$$(A3 + A2' + A1' + A0')$$

0 | 1 | 1 | 1

③ B2 as a sum of products (SOP)

$$B2 = A3 \cdot A2' + A3' \cdot A2$$

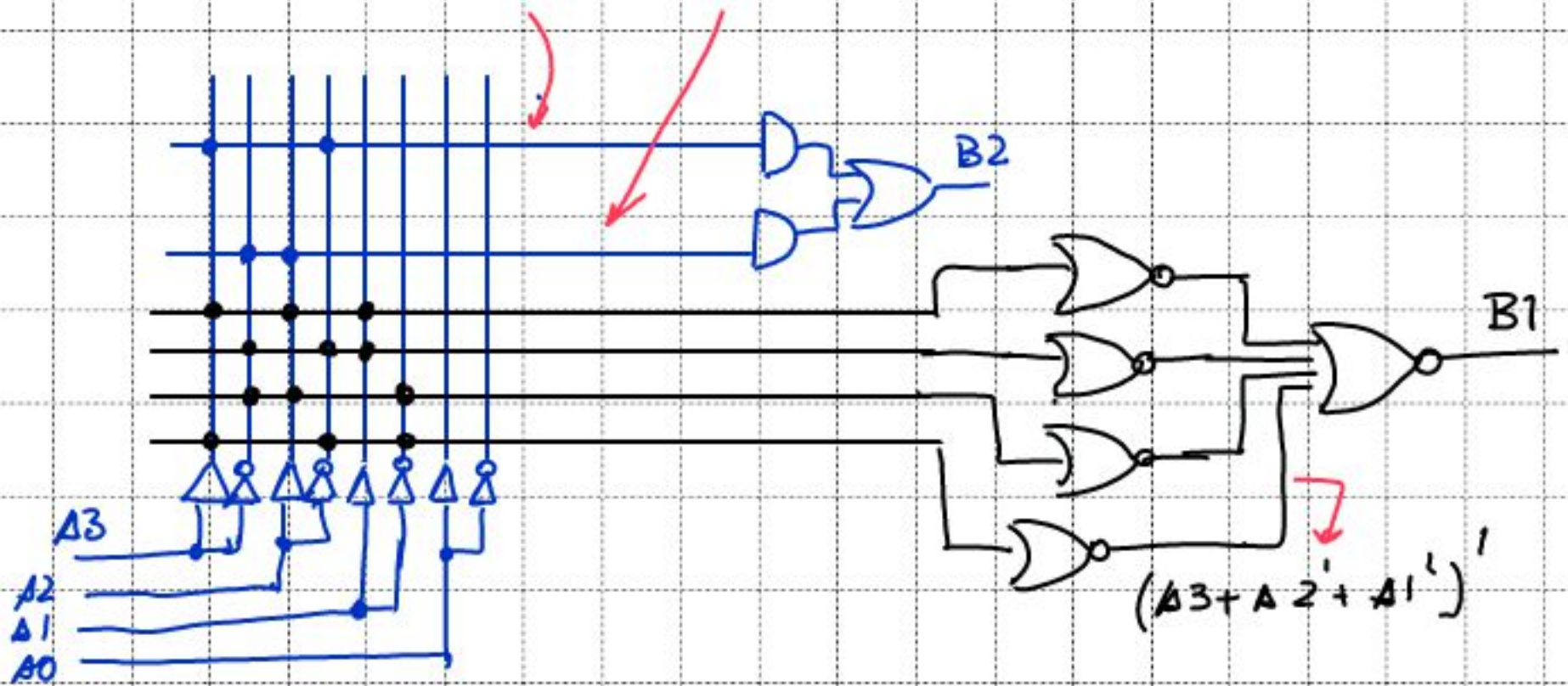

④ B1 as a product of sums (PoS)

$$B1 = (A3 + A2 + A1)' (A3' + A2' + A1)' (A3' + A2 + A1)' (A3 + A2' + A1)'$$

$$(x \cdot y \cdot z \cdot w)'' = (x' + y' + z' + w')$$

$$B1 = ((A3 + A2 + A1)' + (A3' + A2' + A1)' + (A3' + A2 + A1)' + (A3 + A2' + A1)')'$$


Let's check, for instance $A = "1010"$

$$\begin{aligned}
 B1 &= ((1 + 0 + 1)' + (1' + 0' + 1)' + (1' + 0 + 1)' + (1 + 0' + 1)')' \\
 &= (0 + 0 + 1 + 0)' = 0 \quad \text{OK } \checkmark
 \end{aligned}$$

$$\textcircled{5} \quad B_1 = \prod_4 M(0, 1, 6, 7, 12, 13, 10, 11)$$

When $E_L = 0$ $B_2 = \prod_4 M(0, 1, 3, 2, 12, 13, 15, 14)$

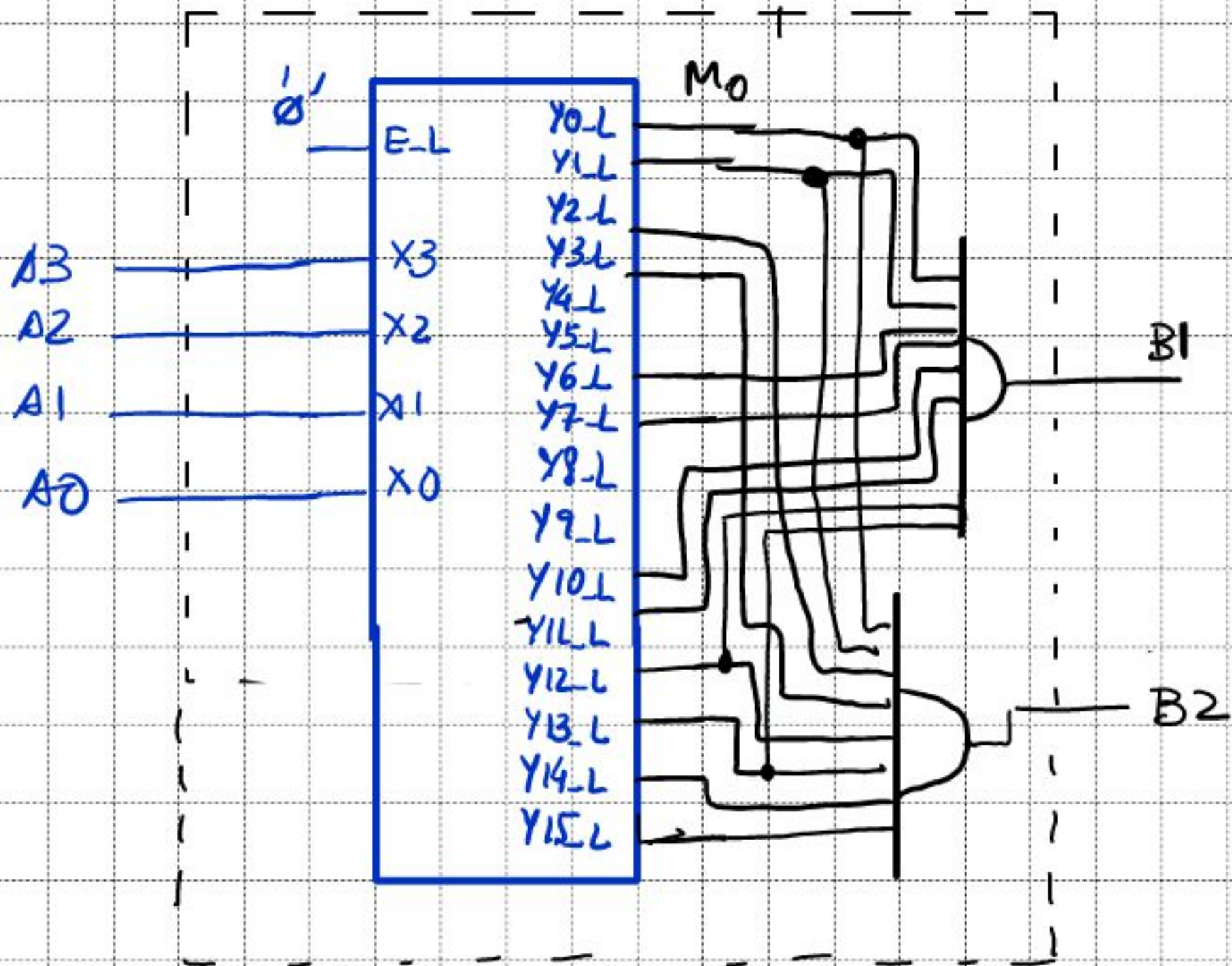↳ The outputs of the decoder are the masterns




$\textcircled{6}$ Because every output of the decoder is a simple mastern

$$Y_{10-L} = (E_L + X_3 + X_2 + X_1 + X_0)$$

$$Y_{10-L} \Leftarrow E_L \text{ or not } (X_3) \text{ or } X_2 \text{ or not } (X_1) \text{ or } X_0;$$

and so the other 15 equations

⑦ It is like the P-Chip

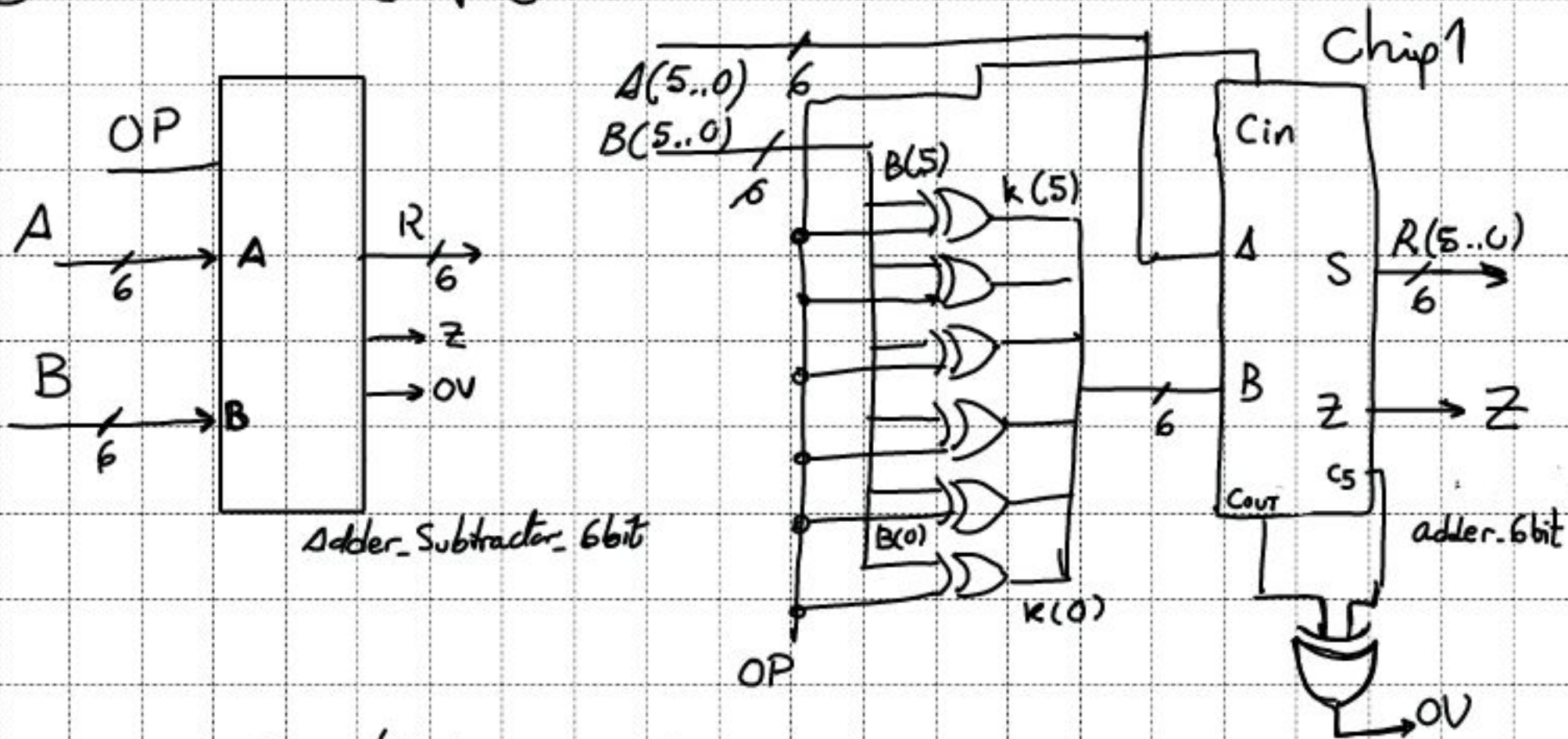

$$Z = (R(5) + R(4) + R(3) + R(2) + R(1) + R(0))'$$

only when the $R=0 \rightarrow Z=1$

$$OV = C5 \oplus Cout \text{ when the carry of the two last sections is different } \rightarrow OV=1$$

$$N = 6 \text{ bit} \rightarrow -2^5 \leq A, B, R \leq 2^5 - 1$$

This is the integer range

$$-32 \leq A, B, R \leq +31$$

⑧ a) $+26 = 011010$
 $OP = 0$
 $B = 101010$
 $\leftarrow 000100$
 $+4$

$$26 + (-22) = +4$$

$$\begin{array}{r} 101010 \\ 010101 \\ \hline 010110 \end{array} \xrightarrow{+22}$$

$$Z = 0$$

$$OV = 0$$

b) $A = -22$
 $B = -21$
 $OP = 1$

$$\begin{array}{r} 101010 \\ + 010101 \\ \hline 111111 \\ \downarrow -1 \\ 000000 \\ +1 \\ \hline 000001 \end{array} \rightarrow 1$$

$$\begin{array}{r} 010101 \\ + 1 \\ \hline 010110 \rightarrow 22 \\ -22 - (-21) = -1 \end{array}$$

$$Z = 0$$

$$OV = 0$$

$$010101 \rightarrow +21$$

$$101010$$

$$\hline 101011$$

c) $A = +18$ $B = -18$ $OP = 0$

$$\begin{array}{r} 010001 \\ + 101110 \\ \hline 100000 \end{array}$$

$R = 0$
 $Z = '1'$
 $OV = '0'$

$$\begin{array}{r} 010001 \\ + 1 \\ \hline 010010 \\ \rightarrow +18 \end{array}$$


d) $A = -31$ $B = +22$ $OP = 1$

$$\begin{array}{r} 100001 \\ + 101010 \\ \hline 001011 \end{array}$$

$\rightarrow XOR \rightarrow OV = 1$

$$\begin{array}{r} +31 \Rightarrow 011111 \\ + 100000 \\ \hline 100001 \end{array}$$
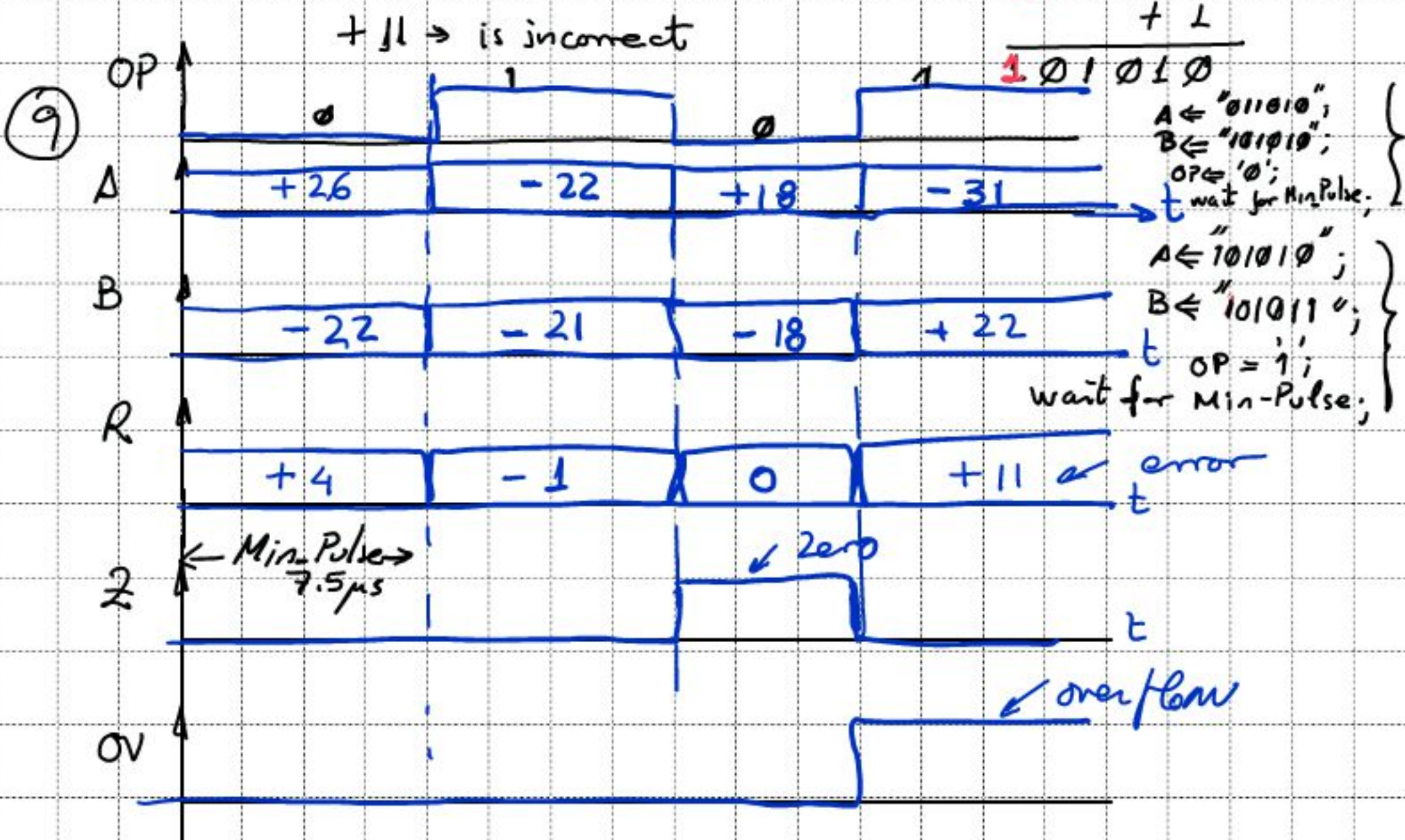
$$\begin{array}{r} +22 \Rightarrow 010110 \\ + 101001 \\ \hline 101010 \end{array}$$



⑩ one way to calculate the speed of the circuit is supposing that the Adder-6bit is a flat structure of 3 level of gates

BUFFER 6ns XOR 6ns ADDER-6BIT 18ns (XOR or NOR) 6ns $\rightarrow P_d = 36ns$

$\Rightarrow f_{max} \leftarrow 27.8 \text{ MHz}$