

**Exam 1**

**April 5, 2019**

**Problem 1. (Option A)**

**2.5p**

Given de following logic function:  $Y = f(a, b, c, d) = a \cdot b + c' + a \cdot c \cdot d$

- a) Express the function using only 2-input NAND. Draw the equivalent logic circuit.
- b) Express the function as a product of maxterms and represent its truth table.
- c) Implement the logic function with the method of decoders (MoD).
- d) Implement the logic function with the method of multiplexers (MoM) and a MUX4.

**Problem 1. (Option B)**

**2.5p**

- a) Deduce the equation that exactly corresponds to the circuit  $Q = f(S1, S0, A, B)$  represented in Fig. 1.
- b) Deduce the circuit's truth table using Boole's Algebra.
- c) If the circuit's logic gates are LS-TTL technology, with a propagation delay of 10 ns, calculate the maximum speed of computing.

 


Fig. 1  
Combinational circuit based on logic gates.

**Problem 2.**

**2.5p**

In the Fig. 2 there is the RTL view of a synthesized circuit obtained with Quartus II in the target chip Cyclone III.

- a) Justify if it is a flat or a hierarchical design. How many VHDL files the project contains?
- b) Draw the symbol of the top entity, naming all the input and output ports.
- c) Draw the truth table of the top entity and indicate how many minterms and maxterms has the output Y.
- d) Draw the architecture of this top entity using the plan A (equations) and represent the logic circuit.

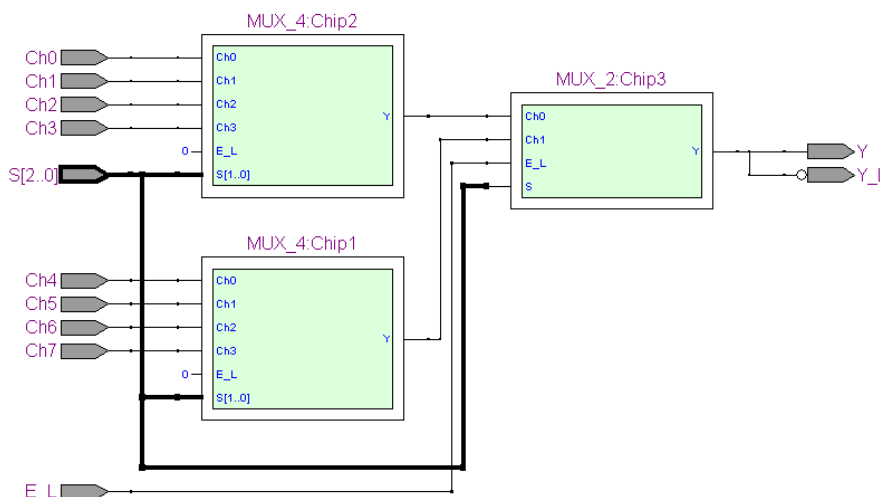


Fig. 2  
RTL view from the EDA synthesizer tool.

Target chip  
Cyclone III.  
3C16F484C6N

**Problem 3.**

**2.5p**

The Fig. 3 represents a timing diagram for a functional simulation of the *Integer\_comp\_8bit* comparator when  $N = 0$  and so, the data is unsigned in radix 2.


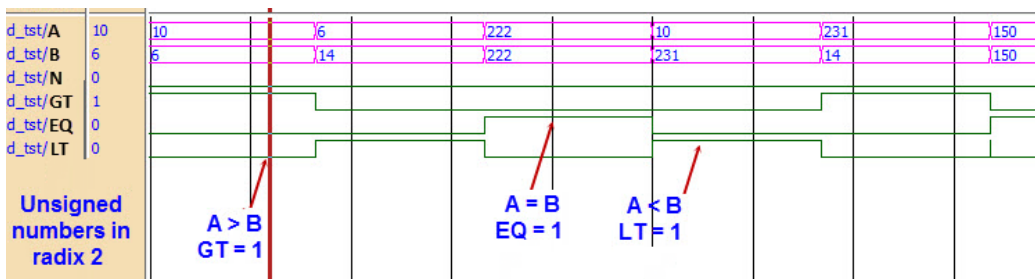


Fig. 3  
Timing diagram of a functional simulation for the circuit represented below:

 

- Draw some values of the truth table of the circuit calculating the outputs for the input stimulus in Fig. 3.
- Represent a similar timing diagram deducing the outputs suposing that now the same **A** and **B** input combinations in '0' and '1' represents data in signed decimal (two's complement) and **N** = '1'.
- Propose a hierarchical internal design of the circuit in Fig. 3 based on simpler chips of the same kind.
- Explain how does the *Comp\_1bit* works (truth table) and how many maxterms has its output GT.

**Problem 4.**

**2.5p**

The Fig. 4 shows the symbol of an 8-bit adder/subtractor which operates two's complemented data.

 


Fig. 4  
Symbol for the *Adder\_subtractor\_8bit*

- Indicate the binary combinations and their equivalent signed decimal results of the following operations. Indicate as well the value of the flags Z, OV and S.
  - $A = 01010101, B = 01110011, OP = 0$
  - $A = 01010101, B = 01110011, OP = 1$
  - $A = 10101111, B = 01111100, OP = 0$
- Invent an internal architecture of this circuit based in plan C2 (hierarchical). Indicate component names, chip references and signals involved.
- Which condition has to be met in order to detect overflow (OV)? Which is the way to solve it using gates?
- Accordingly to the results from the gate-level simulation presented in the Fig. 5, calculate the maximum speed of operation of the *Adder\_Subtractor\_8bit* and the propagation delay of a single gate for this technological implementation.

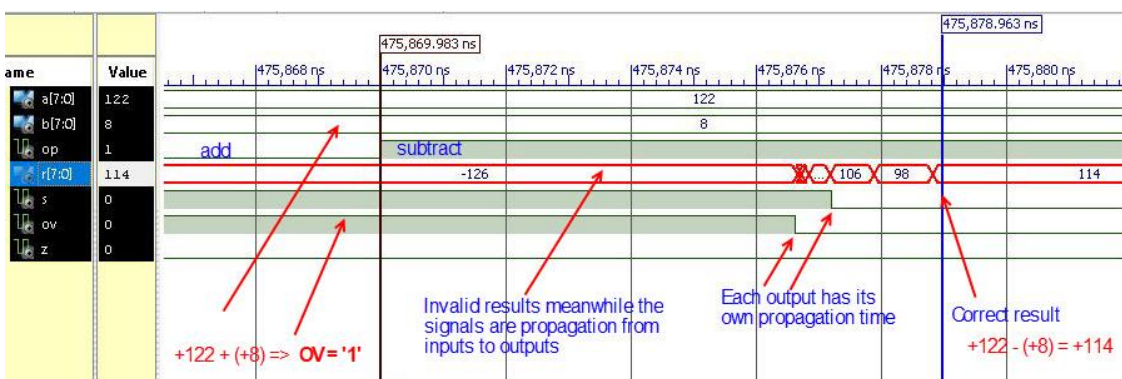


Fig. 5  
Example of gate-level simulation and analysis of the 8-bit adder and subtractor in a given signal transition.

