

Chapter 3 questions

- Use the TMR0 in 16-bit mode of operation (shown in Fig. 2) for designing a frequency meter instrument for measuring unknown frequencies up to 5 MHz. The gate time $T_G = 50\text{ ms}$, when the counter is enabled, is derived from an external signal. Discuss the specifications and propose a plan including hardware and software schematics and diagrams.

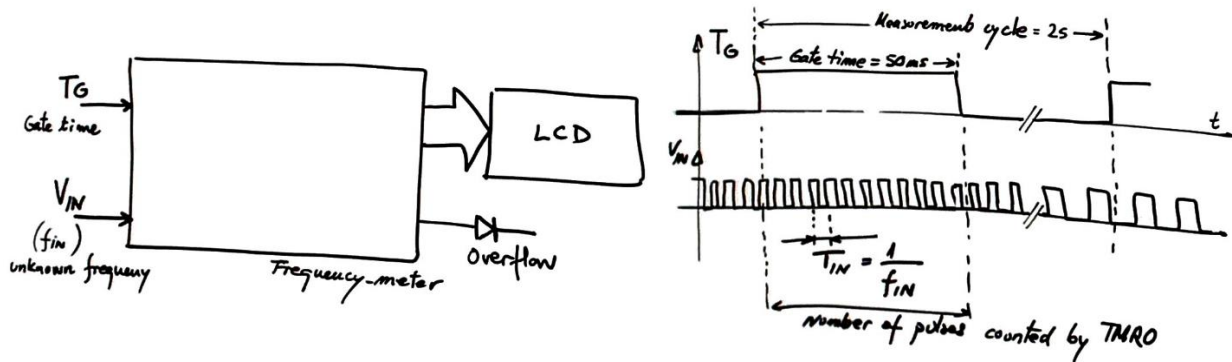


Fig. 1.

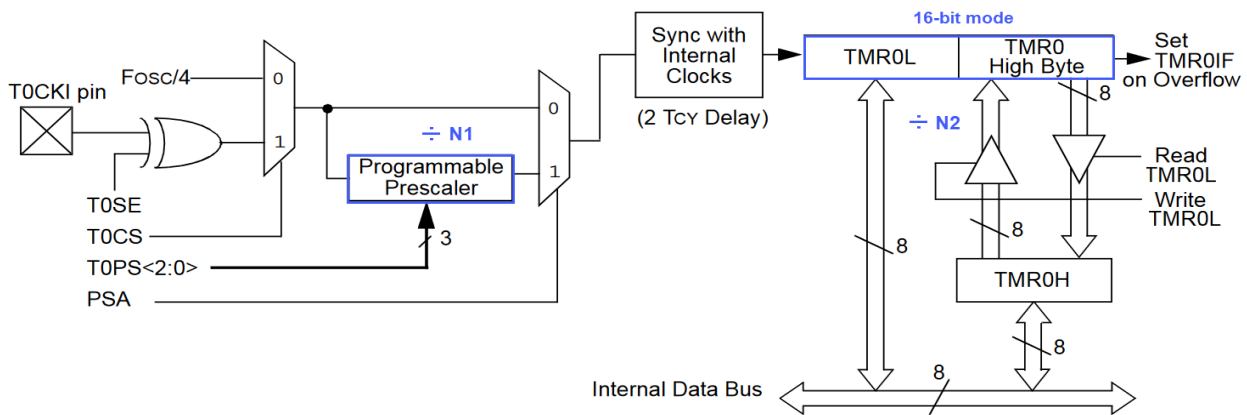


Fig. 2.

- Add to the previous frequency meter an LCD display to show the measured frequency and messages to indicate overflow. Explain what hardware and software modifications are required.
- Use TMR2 peripheral represented in Fig. 3 to replace the external gate time $T_G = 50\text{ ms}$ pulse in Fig. 1. Explain how to plan and organise the software and what functions are affected. $F_{OSC} = 12\text{ MHz}$.

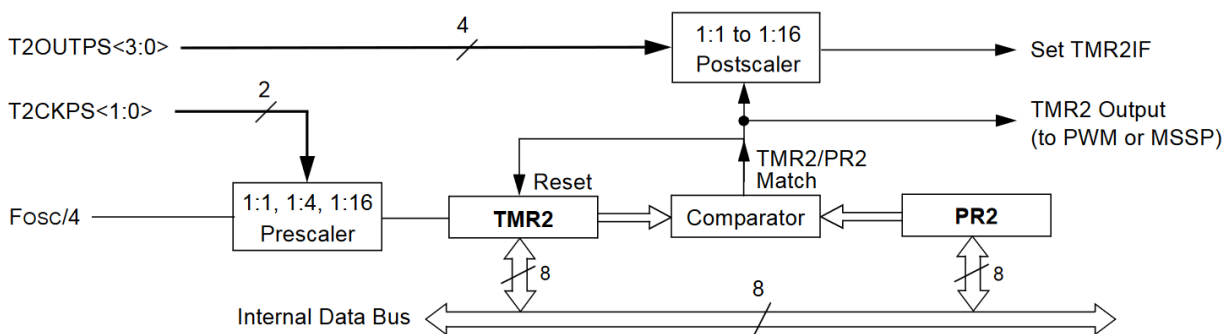


Fig. 3.

4. Read the pins display minutes (DM) and display seconds (DS) of the application represented in Fig. 4 connected at RC6 and RB3 respectively. Explain the flowchart and how are evolving variable content using bitwise operations. Draw and explain what is a power-on reset circuit and how does it work.

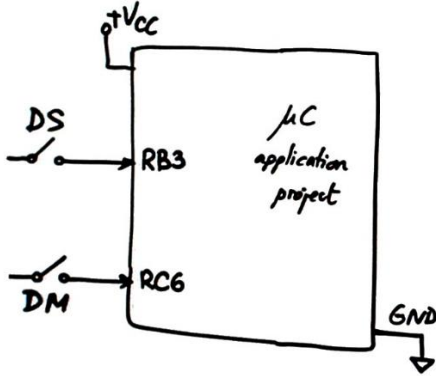


Fig. 4.


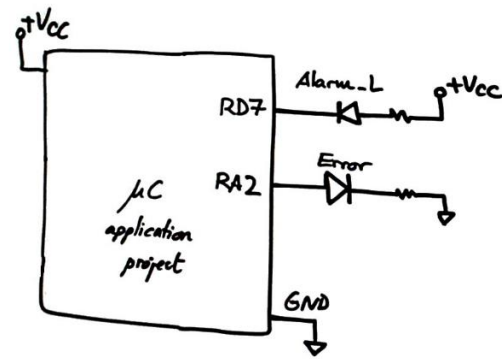


Fig. 5.

5. Write the variables `var_Alarm` and `var_Error` in the pins indicated in Fig. 5. Explain the flowchart of bitwise operations and the memory content while preserving the port bits of no interest. Draw and explain what is a typical circuit for a microcontroller oscillator and why it is required.

Chapter 2 questions

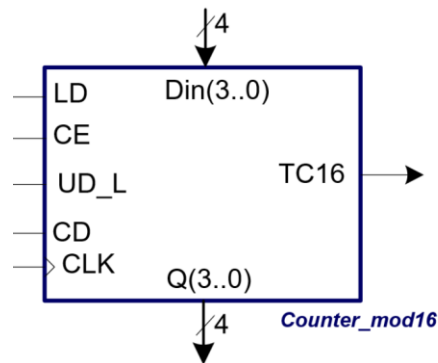6. Invent a synchronous BCD down counter module 13 (`Counter_BCD_mod13`) using plan C2 and the universal component `Counter_mod16` the symbol of which is proposed in Fig. 6. Specifications (symbol, timing diagram, state diagram) and plan (schematics and components).



LD	CE	UD_L	Q*	Synchronous operation after the CLK's rising edge
1	x	x	Din	Parallel load (register data)
0	0	x	Q	Do nothing (inhibit)
0	1	1	$(Q+1)_{mod16}$	Up counting in binary
0	1	0	$(Q-1)_{mod16}$	Down counting in binary

TC16 = '1' when CE = '1' and $[(Q = 15 \text{ and } UD_L = '1') \text{ or } (Q = 0 \text{ and } UD_L = '0')]$; '0' otherwise

Fig. 6.

7. Using our FSM or dedicated processor strategies, invent a digital door lock as represented in Fig. 7 that opens a door (CNTL = '1') only when the secret code "65" is detected. Specifications (symbol, timing diagram, state diagram) and plan. Determine the number of VHDL files required.

 


Fig. 7.

8. Invent the synchronous *CLK_generator* represented in Fig. 9. Specifications and plan. Number of *D_FF* used. Number of VHDL files included in the project. Design a *Freq_div_N* using plan Y.

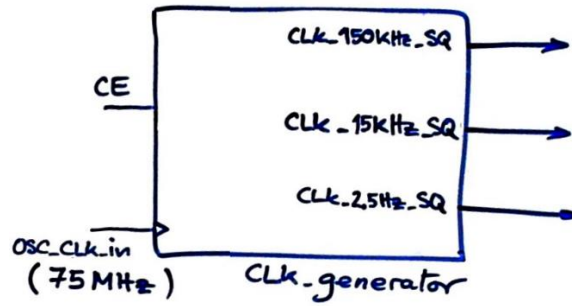


Fig. 8.

9. Invent a 10-bit universal shift register using plan C2 and the component represented in Fig. 9. Use the invented device to generate a 10-bit LED left rotator in one-hot code.

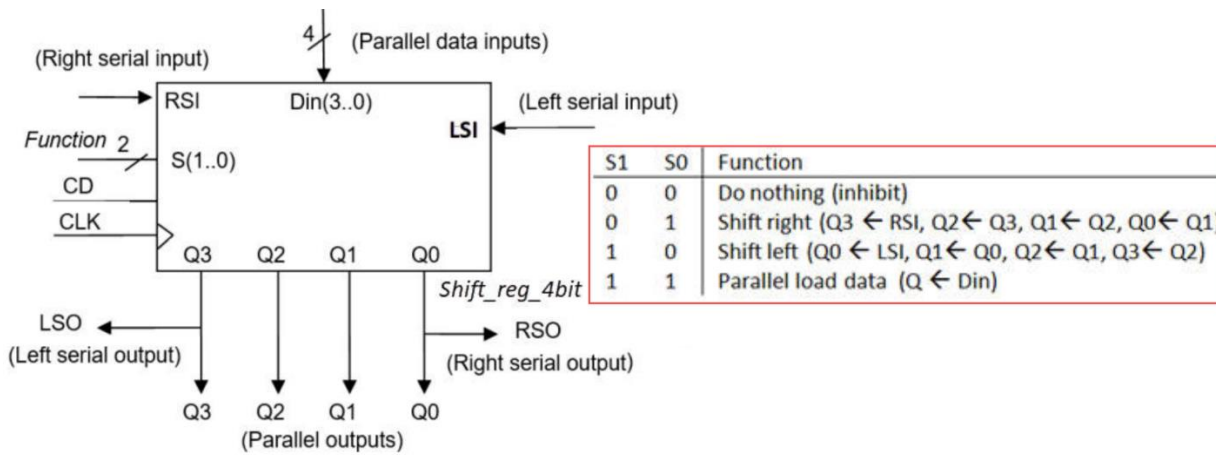


Fig. 9.

10. Analyse the circuit in Fig. 10 using a timing diagram and find the binary codes in the output vector $Q(2..0)$. Discuss what will be the circuit's maximum frequency of operation, and how to measure it in the laboratory.

 


Fig. 10.