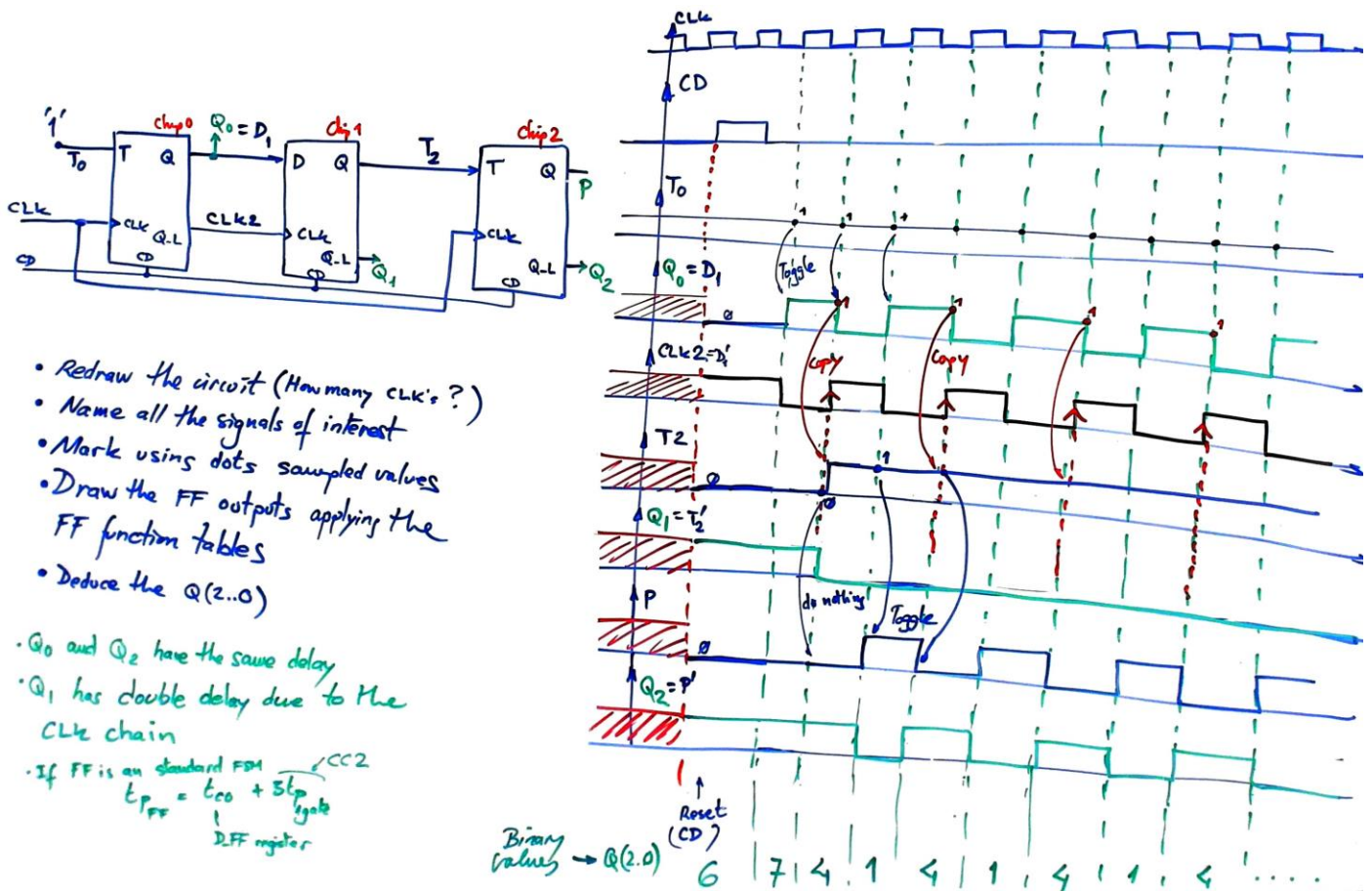


**Problem 1. P5, LAB5:** On the use of FF, asynchronous circuits (this is the circuit in [Proteus](#))



- Redraw the circuit (How many CLK's?)
- Name all the signals of interest
- Mark using dots sampled values
- Draw the FF outputs applying the FF function tables
- Deduce the Q(2..0)
- Q0 and Q2 have the same delay
- Q1 has double delay due to the CLK chain
- If FF is an standard FDM  $t_{PF} = t_{CO} + 5t_{gate}$  (CC2) 2FF register

**Problem 2** [P9, LAB9](#): basic I/O and software organisation.

**Problem 3** [P7, L7.3](#): counter truncation and chaining

**Problem 4** [D2.5 – D3.5](#) Electronic LED dimmer, Johnson generator, 1-bit sequencing

**Problem 5** [D2.23 – D3.23](#) earbuds, touch sensor, click pattern sampling and decoding

**Problem 6** [D2.6 - D3.6](#) LED pattern or 7-segment sequencer, start/stop button